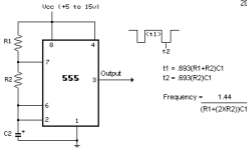


Basic Astable Circuit


Brought to you by:
TOM CAT
DOMAIN BBS
208-375-6571



Here pins 2 and 6 are connected so the circuit will trigger itself each timing cycle, thereby functioning as an oscillator. C1 charges through R1 and R2 but discharges through R2. The charge on C1 ranges from $\frac{1}{3} V_{cc}$ to $\frac{2}{3} V_{cc}$. The oscillation frequency is independent of Vcc.

Bouncefree Switch

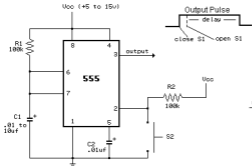
Brought to you by:
TOM CAT
DOMAIN BBS
208-375-6571



C1 (uF)	Delay (seconds)
.1	.01
1	.1
10	1.0

Event Failure Alarm

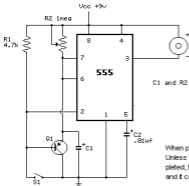Brought to you by
TOM CAT
DOMAIN BBS
208-375-8571




$C1$ and $R2$ control delay

When power is applied, $C1$ starts to charge through $R2$. Unless $S1$ is closed BEFORE the timing cycle is completed, the buzzer will sound. Use any switch for $S1$ and it can be mounted externally from the circuit.

$Q1=2N3906$ $C1=2.2\mu f$ to $47\mu f$

Inside of 555 Timer Chip

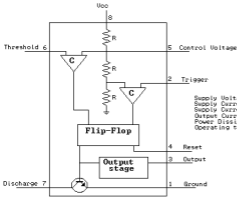Brought to you by:
TOM CAT
DOMAIN BBS
208-375-6571




C = Comparator

Supply Voltage (V_{cc})=4.5 to 15v
Supply Current ($V_{cc}=5v$)=3 to 6 ma
Supply Current ($V_{cc}=15v$)=10 to 15 ma
Output Current = 200ma Maximum
Power Dissipation 600mw
Operating temp. 0 to 70 degrees C

Light/Dark Detector

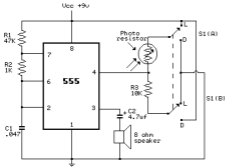
Brought to you by:
TOM CAT
DOMAIN BBS
208-375-6571



$R1$ and $C1$ determine frequency of tone. When $S1$ is in "L" position the speaker will emit a tone when the photo resistor is struck by light. When $S1$ is in "D" position the speaker will emit a tone when photo resistor is NOT illuminated.

LED Flasher

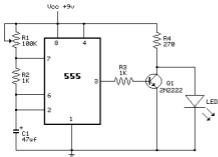
Brought to you by
TOM CAT
DOMAIN BBS
208-375-6571



R1	Rate (Hz)
100K	.2
47K	.6
22K	1.1
10K	2.1
4.7K	3.6
2.2K	6.1
1.0K	8.3

Basic Monostable Circuit

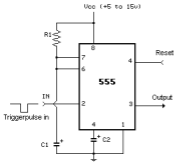Brought to you by:
TOM CAT
DOMAIN BBS
208-375-6571



A negative trigger pulse at Pin 2 turns off a transistor that otherwise shorts C1 to ground, the output then goes high as C1 charges through R1. When the charge on C1 is $\frac{2}{3} V_{cc}$ the 555 discharges C1 to ground. The output then goes low.

Make reset and trigger momentarily low to reset timing cycle. Otherwise keep reset at Vcc.



$$T = R1 \times C1$$

T is independent of Vcc


T = Time in seconds

R = Resistance in Ohms

C = Capacitance in Farads

Timer Operated Relay

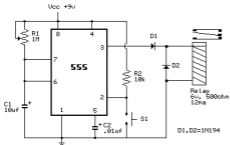
Brought to you by:
TOM CAT
DOMAIN 885
208-375-6571



Closing S1 will start the timing cycle. The relay will be activated during the timing cycle. C1 and R1 control the time delay. C2 prevents triggering, D2 absorbs the energy generated when the relay coil is switched off.

R1	C1=10µf	C1=100µf	
100k	2	16	Approximate delay times in seconds
220k	8	33	
470k	6	70	
1M	15	175	

Toy Organ

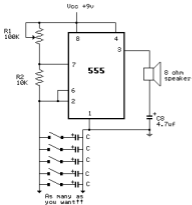


Brought to you by:
TOM CAT
DOMAIN BBS
208-375-8571

C (uf)	Frequency (Hz)
.22	52
.15	79
.1	111
.068	170
.047	230
.033	348
.022	490
.015	718
.01	1,173
.0068	1,679
.0047	2,248
.0033	3,152
.0022	4,671
.0015	6,936
.001	9,237

Variable Frequency Pulse Generator

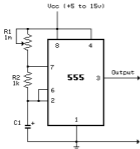Brought to you by:
 TOM CAT
 DOMAIN 885
 208-375-6571



C1=.002 to 1uf

C1	R1=10k	R1=100k	R1=1M
.002	42,478	5,240	520
.005	98,456	12,740	1271
.01	21,522	2,638	261
.02	16,909	1,987	197
.05	11,522	1,414	140
.1	7,210	879	87
.2	4,959	601	60
.5	3,530	428	42
1	2,851	285	28
2	1,787	178	17
5	1,139	113	11
10	694	69	6
100	240	24	2

FREQUENCIES